

EARL JOHN MASAGA

Methodology of an 8 x 3 Encoder.

1. For the 7805-voltage regulator the pin1 should be connected to the source, pin2 should be connected to the ground.
2. For the 7 buttons each input pin should be connected to the pin3 of 7805-voltage regulator.
3. For the 7 1K OHM resistors it must be connected between each of the output pin of the buttons and to the ground.
4. For the 1<sup>st</sup> OR gate, the 1<sup>st</sup> input pin should be connected to the output pin of the 7<sup>th</sup> button and the 2<sup>nd</sup> input pin should be connected to the output pin of the 6<sup>th</sup> button.
5. For the 2<sup>nd</sup> OR gate, the 1<sup>st</sup> input pin should be connected to the output pin of the 5<sup>th</sup> button and the 2<sup>nd</sup> input pin should be connected to the output pin of the 4<sup>th</sup> button.
6. For the 3<sup>rd</sup> OR gate, the 1<sup>st</sup> input pin should be connected to the output pin of the 1<sup>st</sup> OR gate and the 2<sup>nd</sup> input pin should be connected to the output pin of the 2<sup>nd</sup> OR gate.
7. For the 4<sup>th</sup> OR gate, the 1<sup>st</sup> input pin should be connected to the output pin of the 7<sup>th</sup> button and the 2<sup>nd</sup> input pin should be connected to the output pin of the 6<sup>th</sup> button.
8. For the 5<sup>th</sup> OR gate, the 1<sup>st</sup> input pin should be connected to the output pin of the 3<sup>rd</sup> button and the 2<sup>nd</sup> input pin should be connected to the output pin of the 2<sup>nd</sup> button.

9. For the 6<sup>th</sup> OR gate, the 1<sup>st</sup> input pin should be connected to the output pin of the 4<sup>th</sup> OR gate and the 2<sup>nd</sup> input pin should be connected to the output pin of the 5<sup>th</sup> OR gate.
10. For the 7<sup>th</sup> OR gate, the 1<sup>st</sup> input pin should be connected to the output pin of the 7<sup>th</sup> button and the 2<sup>nd</sup> input pin should be connected to the output pin of the 5<sup>th</sup> button.
11. For the 8<sup>th</sup> OR gate, the 1<sup>st</sup> input pin should be connected to the output pin of the 3<sup>rd</sup> button and the 2<sup>nd</sup> input pin should be connected to the output pin of the 1<sup>st</sup> button.
12. For the 9<sup>th</sup> OR gate, the 1<sup>st</sup> input pin should be connected to the output pin of the 7<sup>th</sup> OR gate and the 2<sup>nd</sup> input pin should be connected to the output pin of the 8<sup>th</sup> OR gate.
13. For the 10<sup>th</sup> AND gate, the 1<sup>st</sup> input pin should be connected to the output pin of the 9<sup>th</sup> AND gate and the 2<sup>nd</sup> input pin should be connected to the output pin of the 3<sup>rd</sup> NOT gate.
14. For the 3 LED each positive pin should be connected to the output pins of our OR gates. These are 3<sup>rd</sup>, 6<sup>th</sup> and lastly the 9<sup>th</sup> OR gate. And for the negative pin of the LEDS each should be connected to the ground.
15. Conduct functionality test.